

PHSA (HN)-07(A)

West Bengal State University
B.A./B.Sc./B. Com. (Honours, Major, General) Examinations, 2015

PART - III
PHYSICS — HONOURS
PAPER - VII-A

Duration : 2 Hours]

[Maximum Marks : 50

Candidates are required to give their answers in their own words as far as practicable.

The figures in the margin indicate full marks.

Answer Question No. 1 and any four from the rest.

Answer any five questions :


5 × 2 = 10

1. a) How is a FET used as a voltage variable resistance ?
- b) Design a 4 to 1 multiplexer using basic gates.
- c) What is a multivibrator ?
- d) Explain why negative feedback in amplifier is used widely though it reduces the gain.
- e) Show that current flowing through the feedback resistance of ideal non-inverting amplifier is independent of its value.
- f) Draw the output waveform of a modulo four ripple counter.
- g) Draw the block diagram of an amplifier with negative feedback. Find an expression for its closed loop gain.
- h) If the applied a.c. power to a system is $5\mu\text{W}$ at 100 mV and the output power is 48 W, show that power gain in decibels is 69.83.

SUB-B.Sc. (HN)-PHSA-12084

[Turn over

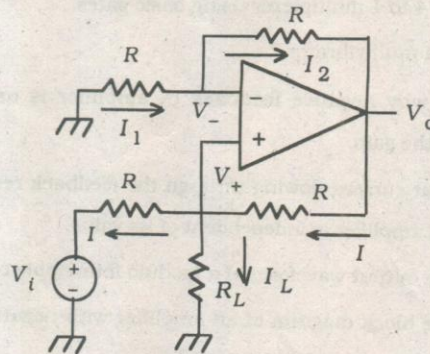2.
 - a) Draw the static drain characteristics of a common source n -channel FET and give corresponding circuit diagram. 2
 - b) What is pinch-off voltage? Draw the nature of depletion region in an n -channel FET (common source) at pinch-off voltage. 1 + 2
 - c) For a JFET write down the relationship between I_D and V_{GS} (in common source configuration). Who discovered it? 1 + 1
 - d) An n -channel FET has $I_{DSS} = 8 \text{ mA}$, $V_P = -4 \text{ volt}$. Find V_{GS} that will result in a drain current of 4.5 mA . 3
3.
 - a) How is linear oscillator different from multivibrator? 2
 - b) State Barkhausen criterion. 2
 - c) Draw the circuit diagram of a Wien-bridge oscillator. Determine its oscillation frequency. 1 + 3
 - d) How is amplitude stabilized in Wien-bridge oscillator? 2
4.
 - a) What is digital comparator? 2
 - b) Design a 1 bit comparator that has two inputs A and B and three outputs, one each for equality, $A = B$, greater than, $A > B$ and less than $A < B$. 4
 - c) What is a shift register? 1
 - d) Draw a block diagram of 3-bit serial in serial out shift register. Draw the output waveform if the input word is 101. 3
5. Assuming ideal Op-Amp characteristics answer the following :



- a) If $I_1 = I_2$
show that $V_- = \frac{V_0}{2}$.


2

b) If $I = I_L + I'$
 show that $V_+ = \frac{(V_o + V_t) R_L}{(R + 2R_L)}$ 3

c) State the principle of virtual ground. Use it to show that
 $\frac{V_o}{V_t} = \frac{2R_L}{R}$ 3

d) Draw the circuit diagram of a half-wave rectifier, where the peak value of input sinusoid is 0.1 mV. 2

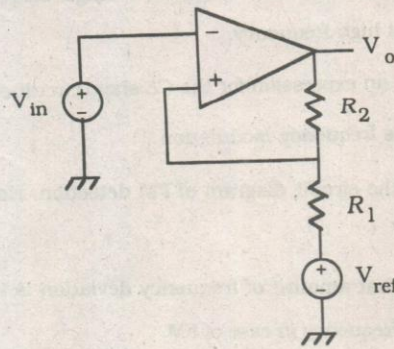6. a) What is the difference between basic comparator and Schmitt trigger? 2
 b) Assuming ideal Op-Amp characteristics answer the following :



Show that $V_{TU} = V_C + V_H \frac{R_1}{R_1 + R_2}$

$V_{TL} = V_C + V_L \frac{R_1}{R_1 + R_2}$

where $V_C = V_{ref} \frac{R_2}{R_1 + R_2}$

$V_H = +V_{supply}$

$V_L = -V_{supply}$

V_C = Centre voltage, V_{TU} and V_{TL} are upper and lower threshold voltages respectively. 3

- c) Explain why a quartz crystal is widely used in the design of sinusoidal oscillators ? 1
- d) Draw the electrical model of a quartz crystal.
Sketch the reactance vs frequency function.
If the crystal has the following parameters :
 $L = 0.33 \text{ H}$, $C = 0.065 \text{ pF}$, $C' = 1.0 \text{ pF}$,
 $R = 5.5 \text{ K}$, find series resonance frequency and Q of the crystal. 1 + 1 + 2
7. a) Draw the equivalent circuit for a single stage CE amplifier with resistive load at high frequency. 2
- b) Derive an expression for the CE short circuit current gain. 3
- c) What is frequency modulation ? 1
- d) Draw the circuit diagram of FM detection. How is bandwidth defined in FM ? 2
- e) Show that amount of frequency deviation is independent of modulating signal frequency in case of FM. 2
-